

Post-Session:

- (i) Compute the expected DC voltages in your amplifier circuit using the measured β value and compare with your observations.
- (ii) Calculate the small signal mid-band gain with and without the bypass capacitor and compare with your observations.
- (iii) Explain the clipping levels that you have observed in the output waveform.