

## BJT Biasing Circuits


### Theory:

In a BJT amplifier, biasing (i.e., ensuring certain DC values of  $I_C$ ,  $V_{CE}$ , etc) is very important for two reasons:


- The DC bias point has a direct impact on the maximum swing that can be obtained at the output pin.
- The DC collector current  $I_C$  also determines the transconductance  $g_m$  of the BJT since  $g_m = \frac{I_C}{V_T}$ ,  $V_T$  being the thermal voltage,  $V_T = \frac{kT}{q}$ , approximately 25 mV at room temperature.

A good biasing arrangement must be insensitive to variation in the gain ( $\beta$ ) of the BJT. This is because  $\beta$  can vary significantly from transistor to transistor (even with the same part number); also  $\beta$  can change appreciably as the device temperature changes.

### Potential divider biasing:

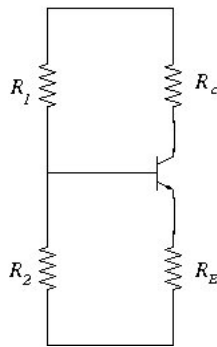

**Figure 1**

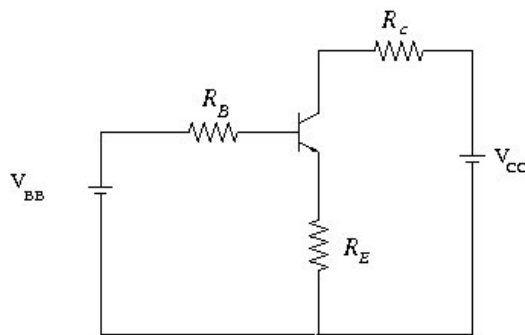

**Figure 2**

A potential divider consisting of  $R_1$  and  $R_2$  (see Fig. 1) can be used to establish the desired DC bias voltage  $V_{BB}$  at the base.

DC analysis:

- Thevenin equivalent of base circuit gives,

$$V_{BB} = \frac{R_2}{R_1 + R_2} \cdot V_{CC}$$

- $R_B = R_1 \parallel R_2$

- Applying KVL to base circuit loop and collector circuit loop we get,

$$V_{BB} = I_B \cdot R_B + I_E \cdot R_E + V_{BE}$$

$$V_{CC} = I_C \cdot R_C + V_{CE} + I_E \cdot R_E$$

Solving we get,

$$I_E = \frac{(V_{BB} - 0.7)(\beta + 1)}{R_B + (\beta + 1)R_E} \text{ where, } V_{BE} = 0.7V$$

- Since  $V_{BB} \gg V_{BE}$ , small variations in  $V_{BE}$  can be swamped by  $V_{BB}$ .

However, if  $V_{BB}$  is made too large, the voltage  $V_{CE}$  gets reduced and that limits the voltage swing. Hence as a rule of thumb while designing the biasing circuit;

$V_{BB}$ ,  $V_{CE}$ , and  $I_C R_C$  are chosen about  $\frac{1}{3} V_{CC}$ .

- $R_E \gg \frac{R_B}{(\beta + 1)}$ .

If  $R_E$  is sufficiently large compared to  $R_B$ , any small variation in  $\beta$  does not affect  $I_E$  and hence  $I_C$  to a large extent. This is achieved by choosing small  $R_B$ . However, if  $R_B$  is made too small, the input resistance of the amplifier is reduced. Typically, current through the potential divider is chosen to be about  $0.1 I_E$  to keep the current drain from power supply minimum.

**Role of  $R_E$ :**  $R_E$  provides negative feedback and stabilizes  $I_E$  and hence  $I_C$ . Any increase in  $I_E$  raises the emitter voltage  $V_E$  reducing base emitter forward bias. This reduces base current  $I_B$  and in turn  $I_C$  and hence  $I_E$ .