

## BJT Small-Signal Parameters

**Objectives:** To obtain some small signal parameters of Bipolar Junction Transistors (BJTs).

**Background:** One of the most important applications of BJTs is in amplifiers, where a small input signal is amplified into a large output signal. For such applications, the small-signal (linear) parameters of a transistor are more important than the DC I-V characteristics which were measured in Experiment No.6. To analyze a BJT amplifier circuit, it is convenient to replace the transistor when it is in the *linear* region by its “small-signal equivalent circuit”. There are many equivalent circuits in use for BJTs, and one of the most common is the (common-emitter) hybrid- $\pi$  equivalent circuit. In its full form, this is shown in fig 1(a). At low frequencies, and because  $r_{b'e}$  is very large, the equivalent circuit of Fig 1 (b) is often used.

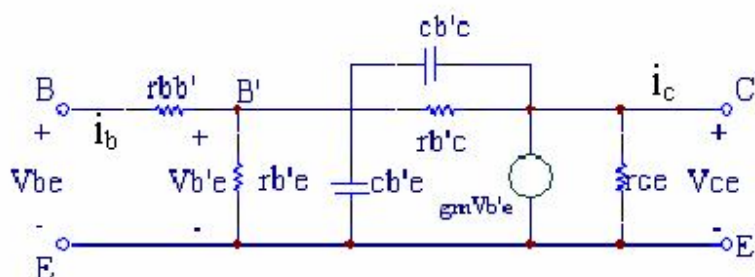


Fig 1(a)

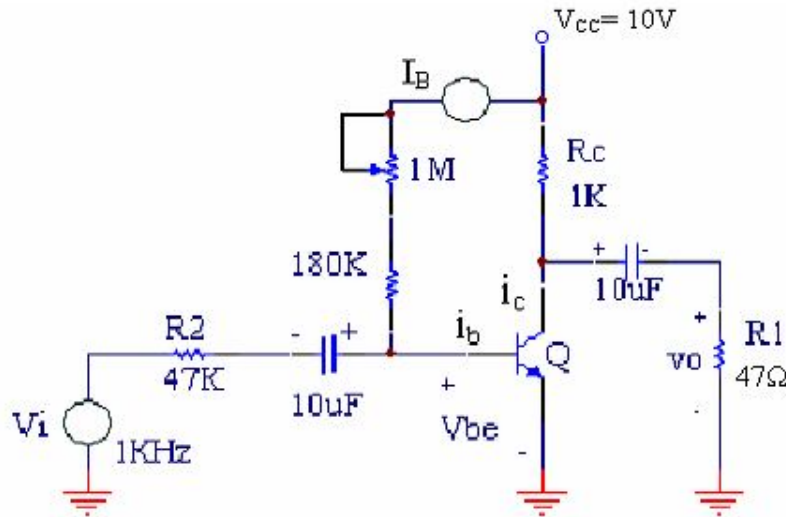


Fig 1(b)

In the circuit of Fig 1 (b),  $r_{bb'}$  and  $r_{b'e}$  together constitute the input resistance ( $r_{bb'}$  is a constant base spreading resistance, whereas  $r_{b'e}$  is the resistance of the B-E junction and goes as  $r_{b'e} = \frac{kT}{qI_B}$ ). The transconductance  $g_m$  represents the gain of the transistor and  $r_{ce}$  is the output

resistance. Sometimes the current source  $g_m v_{b'e}$  is drawn as  $\beta i_b$  with the current gain  $\beta = g_m r_{b'e}$  (show that this is the case).

**Experiment:** The resistances  $r_{bb'}$  and  $r_{b'e}$  can be measured by measuring the small-signal (ac) input resistance as a function of the DC base current  $I_B$  when the output is AC-short-circuited. A possible set up to use is shown in Fig. 2.



**Fig 2**

Use an appropriate value of  $v_i$ , such that  $v_{be}$  is about 20-30 mV peak-to-peak.

Ensure that the transistor is in the active region ( $V_{CE}$  should be in the range 1-9 V). The ac input resistance is given by


$$r_i = r_{bb'} + r_{b'e} = r_{bb'} + \frac{kT}{qI_B} = \frac{v_{be}}{i_b} \approx \frac{v_{be}}{\frac{v_i - v_{be}}{R_2}}$$

(Note: Measure all voltages on the scope, to ensure that they are good sine waves) Measure  $r_i$  for different values of  $I_B$  (in the range approximately 6-50 $\mu$ A) which will enable  $r_{bb'}$  and  $r_{b'e}$  to be extracted. While measuring  $r_i$ , you can also measure the small signal  $\beta$  of the transistor which is given by,

$$\beta = \frac{i_c}{i_b} \approx \frac{v_o / R_1}{i_b}$$

A knowledge of  $\beta$  and  $r_{b'e}$  (both as functions of  $I_B$ ) enables you to find out  $g_m$ .

To find  $r_{ce}$ , the circuit shown in fig.3 can be used. (Note that  $f=10$  KHz in this circuit. Change the value of  $R_0$  till the output voltage becomes half the open-circuit output voltage. Then,  $r_{ce} \approx R_0$ . Measure  $r_{ce}$  as a function of  $I_C$ .

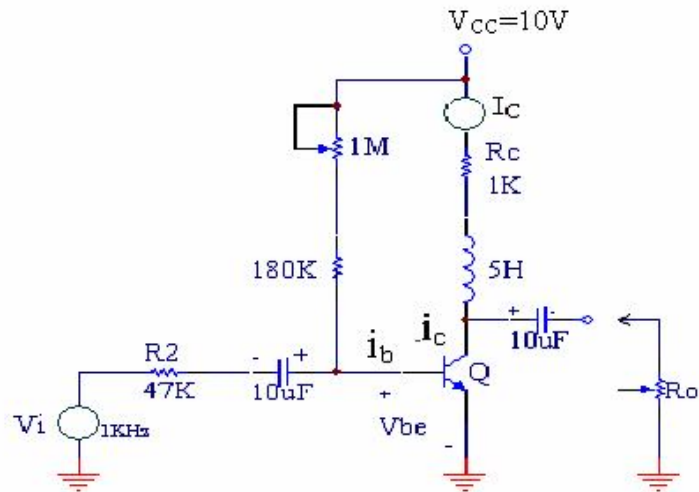

**Figure 3**