

Post-session work:

- (a) Plot r_i versus $1/I_B$. Thus extract out $r_{bb'}$ and $r_{b'e}(I_B)$.
- (b) From the measurement of $r_i(I_B)$ and $\beta(I_B)$, find $g_m(I_B)$.
- (c) Find $r_{ce}(I_C)$.
- (d) Plot g_m v/s I_B . Is it approximately linear?
- (e) Plot r_{ce} versus $1/I_C$. Is it approximately linear? If so, find the Early voltage V_A , defined as the slope of r_{ce} versus $1/I_C$.