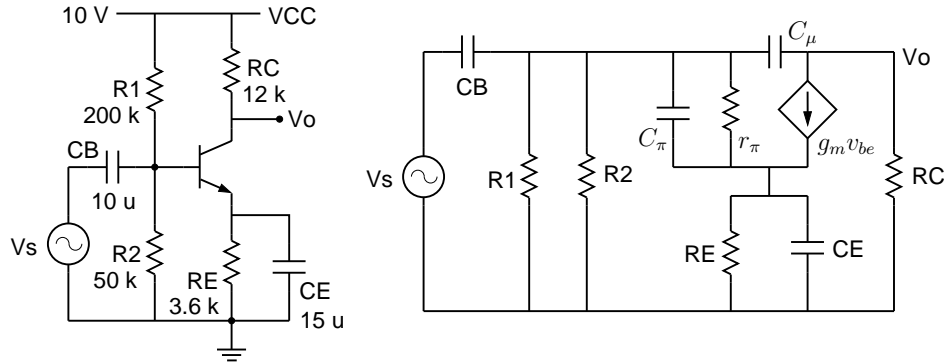


## bjt\_ce\_amp.sqproj

### Description



Shown in the figure is a common-emitter amplifier and its small-signal equivalent circuit. The midband gain of the circuit is given by  $A_V = -g_m R_C$ . The capacitors  $C_B$  and  $C_E$  influence the low cut-off frequency  $f_L$  whereas the device capacitances  $C_\pi$  and  $C_\mu$  influence the high cut-off frequency  $f_H$ .

### Exercise Set

1. For the given component values, calculate the bias current  $I_C$  and the midband gain  $A_V$ . Verify with simulation results.
2. Change  $C_B$  from  $10\ \mu F$  to  $20\ \mu F$ , and observe its effect on  $f_L$ .
3. Change  $C_E$  from  $15\ \mu F$  to  $30\ \mu F$ , and observe its effect on  $f_L$ .
4. The capacitance  $C_\mu$  is directly proportional to the BJT parameter `cjc` (collector junction capacitance at zero bias) [1]. Increase the value of `cjc` by a factor of 2, and observe its effect on  $f_H$ .
5. Perform transient simulation with a  $1\text{ mV}$  sinusoidal input with  $f = 1\text{ kHz}$  and observe the output voltage. Verify that the gain matches with that obtained by AC simulation. Repeat for  $f = 100\text{ Hz}$ .
6. If only a part of  $R_E$  (say,  $3\text{ k}$  out of  $3.6\text{ k}$ ) is bypassed, how will it affect  $I_C$  and  $A_V$ ? Verify with simulation.

## References:

1. P. Antognetti and G. Massabrio, *Semiconductor device modeling with SPICE*, McGraw-Hill: New York, 1988.