

# bjt\_ce\_amp\_2.sqproj

## Description

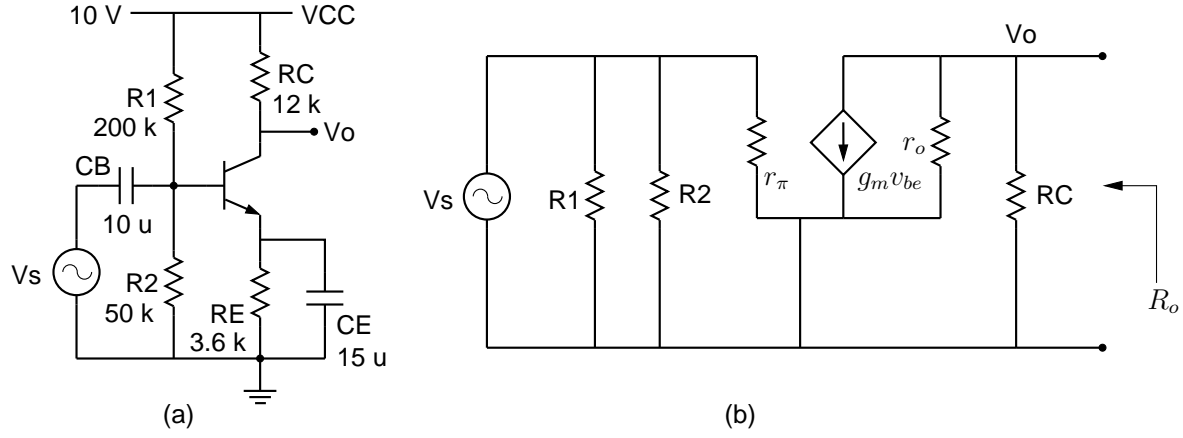


Figure 1: (a) BJT common-emitter amplifier, (b) small-signal equivalent circuit.

The purpose of this exercise is to find the output resistance of a common-emitter amplifier shown in Fig. 1(a) in the mid-band frequency regime. The small-signal equivalent circuit of the amplifier is shown in Fig. 1(b). If the output resistance of the BJT  $r_o$  is large,  $R_o \approx R_C$ . Our goal is to verify this by simulation.

The small-signal circuit of the amplifier can be represented by that shown inside the dashed rectangle in Fig. 2. Let us connect a load resistance  $R_L$  at the output. The output voltage is,

$$v_o = A_V v_s \frac{R_L}{R_o + R_L}. \quad (1)$$

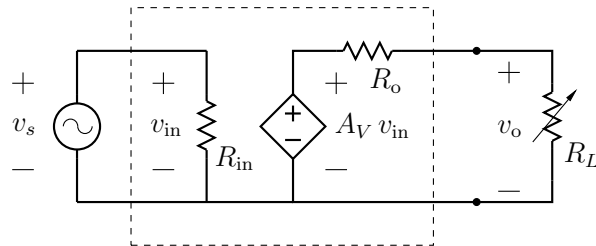


Figure 2: Equivalent representation of the circuit in Fig. 1(b).

If  $R_L \rightarrow \infty$ ,  $v_o \rightarrow A_V v_s$ , and if  $R_L = R_o$ ,  $v_o = A_V v_s/2$ . This gives us the following procedure for finding  $R_o$ :

1. Vary  $R_L$  from  $\infty$  (or a sufficiently large value) to a small value (say, 10 times smaller than the expected value of  $R_o$ ), and plot  $|\mathbf{V}_o|$  versus  $\log R_L$ .
2. Denote the maximum value of  $|\mathbf{V}_o|$  by  $V_m$ . From the plot, find  $R_L$  for which  $|\mathbf{V}_o|$  is  $V_m/2$ . The resistance thus obtained is the same as  $R_o$ .

## Exercise Set

1. Perform DC simulation of the amplifier.
2. Obtain the gain versus frequency response of the amplifier, and find the midband range.
3. Set the frequency in the midband range. Obtain  $R_o$  by simulation, as described above, and compare it with its expected value.